

ENSC350: DIGITAL SYSTEMS DESIGN

SPRING 2024 - 1241

LAB 4: MEMORY, SCHEDULING, AND DECRYPTION

DESCRIPTION

In this lab, you will get experience creating a design that contains several on-chip memories. This is an opportunity to practice what you learned in the lecture on on-chip memory. The circuit you will create is an RC4 Decryption circuit. RC4 is a popular stream cypher, and until recently was widely used in encrypting web traffic among other uses. RC4 has now been deemed insecure and has been replaced by several variants. Still, RC4 is an important algorithm and provides a good vehicle for studying digital circuits that made extensive use of on-chip memory. It also provides a basis for implementing some of these variants that are more secure.

In this lab, you will first design an RC4 decryption circuit. The secret key will be obtained from a bank of switches on your DE2 board, and the encrypted message will be given to you as a ROM initialization file.

- Working week: March 18 – March 22, 2024
- Marking week: March 26 & 28, 2024

BACKGROUND: RC4 DECRYPTION

```
// Input:
//   secret_key [] : array of bytes that represent the secret key. In our implementation,
//                   we will assume a key of 24 bits, meaning this array is 3 bytes long
//   encrypted_input []: array of bytes that represent the encrypted message. In our
//                       implementation, we will assume the input message is 32 bytes
// Output:
//   decrypted_output []: array of bytes that represent the decrypted result. This will
//                       always be the same length as encrypted_input [].

// initialize s array. You will build this in Task 1
for i = 0 to 255 {
    s[i] = i;
}


// shuffle the array based on the secret key. You will build this in Task 2
j = 0
for i = 0 to 255 {
    j = (j + s[i] + secret_key[i mod keylength]) mod 256 //keylength is 3 in our impl.
    swap values of s[i] and s[j]
}

// compute one byte per character in the encrypted message. You will build this in Task 2
i = 0, j = 0
for k = 0 to message_length-1 { // message_length is 32 in our implementation
    i = (i+1) mod 256
    j = (j+s[i]) mod 256
    swap values of s[i] and s[j]
    f = s[ (s[i]+s[j]) mod 256 ]
    decrypted_output[k] = f xor encrypted_input[k] // 8 bit wide XOR function
}
```

This section describes the RC4 decryption algorithm. You can find more information by doing a Google Search, but the information here should be sufficient to complete this lab. Interestingly, the same algorithm is used for both encryption and decryption, but we will only use it for decryption in this lab.

RC4 is a stream cipher. Based on a key, the algorithm generates a series of bytes. Each byte is XOR'ed with one byte of a message to produce the decoded text. The basic RC4 algorithm is shown in the previous page.

The length of the secret key can vary in different applications, but is typically 40 bits (5 bytes). In our implementation, we will assume a 24 bits (3 byte) key for simulation purposes. Note that in the second loop above, `secret_key[0]` refers to the first byte of the key, `secret_key[1]` refers to the second byte of the secret key, and `secret_key[2]` refers to the third byte of the secret key. This is illustrated below; in this example, the 24-bit secret key is `000000110101111100111100 = x035F3C`. The diagram shows how each of `secret_key[0]`, `secret_key[1]`, and `secret_key[2]` are found.

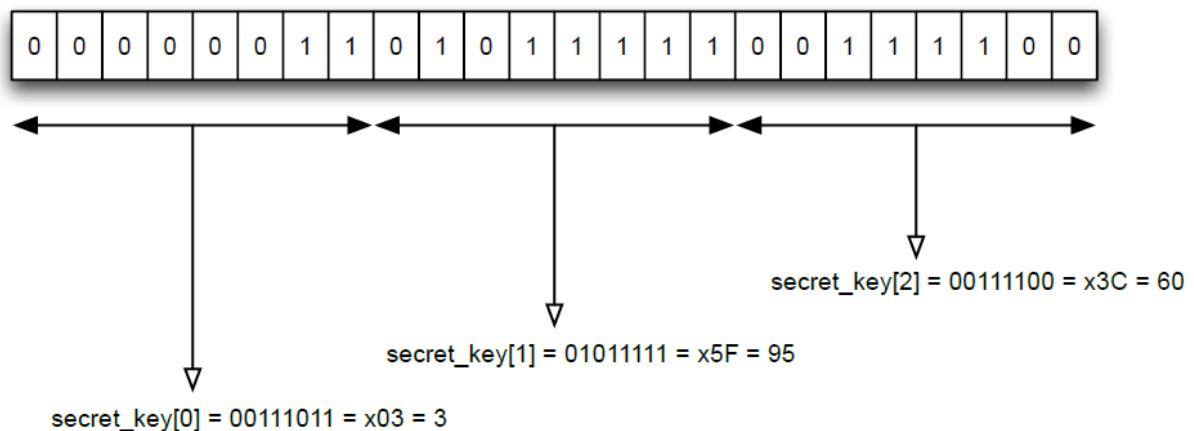

The encrypted message (the input) consists of 32 bytes, and in the above pseudo-code, **encrypted_input[k]** refers to the kth byte in the encrypted input. The decrypted message (the output) will also be 32 bytes; in the above pseudo-code, **decrypted_output[k]** refers to the kth byte in the encrypted output.

Marks

No implementations done in this section; therefore, no marks. However, the information provided must be understood to proceed to the next sections for a correct implementation of the system.

CREATING A MEMORY, INSTANTIATING IT, AND WRITING TO IT

TASK 1: you will get started by creating a RAM using the Wizard in the IP Catalog, creating circuitry to fill the memory, and observing the memory contents using the In-System Memory Content Editor.

Creating a RAM block using the Wizard

First, create a new Quartus II project. Then, choose **Tools->IP Catalog**. In the IP Catalog, select **Basic Functions->On Chip Memory->RAM: 1-Port**. A window Save IP Variation will appear. Modify the file name to be **s_memory.vhd** in your working directory. Hit **OK**. In the next few panels, customize your IP core as follows:

- How wide should the 'q' output bus be? 8 bits
- How many 8-bit words of memory? 256 words
- What should the memory block type be? M9K
- Set the maximum block depth to be: auto words
- What clocking method would you like to use? Single clock
- Which ports should be registered: Make sure 'q' output port is *unselected*
- Create one clock enable signal... : do not select
- Create an 'aclr' asynchronous clear... : do not select
- Create a 'rden' signal... : do not select
- What should the q output be when reading... : New Data
- Get X's for write mask bytes... : selected
- Do you want to specify the initial contents? No
- Allow In-System Memory Content Editor to capture and update.. Select this option
- The 'Instance ID' of this RAM is S
- Generate netlist: do not select
- Output files: select s_memory.cmp (VHDL Component declaration file)
- Do you want to add the Quartus II File to the project? Yes

When you finish this, you will find the file **s_memory.qip** in your project file list. Click on the triangle beside **s_memory.qip** to expand, and you will see **s_memory.vhd**. Open this file and examine it. Near the top of your file, you will find the Entity declaration for **s_memory**, which will look something like this:

```
ENTITY s_memory IS
  PORT
  (
    address      : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
    clock        : IN STD_LOGIC      := '1';
    data         : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
    wren         : IN STD_LOGIC;
    q            : OUT STD_LOGIC_VECTOR (7 DOWNTO 0)
  );
END s_memory;
```

Be sure your declaration matches the above. This is the entity you will include as a component in your design.

Creating a VHDL module that writes to your memory

To get started, examine **ksa.vhd** from the task1 subdirectory in the distribution zip file. You will see that this declares the component that you should have created using the Wizard. Add this file to your project. Examine this file.

You are to add code to implement the following algorithm (this is the very first part of RC4). After the memory is filled, go to a state called DONE that does nothing but stay in DONE (an endless loop).

```


for i = 0 to 255 {
    s[i] = i;
}

```

Import your pin assignments (as usual) and compile. Be sure your design compiles without errors before going on.

Running your code

Download your design and run it as usual. The circuit will fill the on-chip memory with the numbers 0-255. To examine the contents of the memory, you can choose **Tools->In System Memory Content Editor** (while your circuit is running). If you see “No Devices Detected” in the JTAG Chain configuration, select the hardware pulldown and select USB Blaster. This will open a window that shows the memory contents. In the instance manager window (left) you should see a list of memories in your design (in this case, it is only S). Right click S, and choose **Read Data from In-System Memory**.

 

This memory contents will be read and displayed. You should see something like:

Instance 0: S																											
000000	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F	10	11	12	13						
000014	14	15	16	17	18	19	1A	1B	1C	1D	1E	1F	20	21	22	23	24	25	26	27 !"#\$%&'						
000028	28	29	2A	2B	2C	2D	2E	2F	30	31	32	33	34	35	36	37	38	39	3A	3B	() *+, -./0123456789:;						
00003c	3C	3D	3E	3F	40	41	42	43	44	45	46	47	48	49	4A	4B	4C	4D	4E	4F	<=>?@ABCDEFGHIJKLMNO						
000050	50	51	52	53	54	55	56	57	58	59	5A	5B	5C	5D	5E	5F	60	61	62	63	PQRSTUVWXYZ[\]^_`abc						
000064	64	65	66	67	68	69	6A	6B	6C	6D	6E	6F	70	71	72	73	74	75	76	77	defghijklmnopqrstuvw						
000078	78	79	7A	7B	7C	7D	7E	7F	80	81	82	83	84	85	86	87	88	89	8A	8B	xyz{ }~.....						
00008c	8C	8D	8E	8F	90	91	92	93	94	95	96	97	98	99	9A	9B	9C	9D	9E	9F						
0000a0	A0	A1	A2	A3	A4	A5	A6	A7	A8	A9	AA	AB	AC	AD	AE	AF	B0	B1	B2	B3						
0000b4	B4	B5	B6	B7	B8	B9	BA	BB	BC	BD	BE	BF	C0	C1	C2	C3	C4	C5	C6	C7						
0000c8	C8	C9	CA	CB	CC	CD	CE	CF	D0	D1	D2	D3	D4	D5	D6	D7	D8	D9	DA	DB						
0000dc	DC	DD	DE	DF	E0	E1	E2	E3	E4	E5	E6	E7	E8	E9	EA	EB	EC	ED	EE	EF						
0000f0	F0	F1	F2	F3	F4	F5	F6	F7	F8	F9	FA	FB	FC	FD	FE	FF										

As you can see, the memory has been filled. Each location ‘i’ contains the value ‘i’. Be sure that your program has filled the memory as expected. You will use the In-System Memory Content Editor to help you debug your lab in Task 2, so be sure you are able to get this working before moving on.


Marks

This section will have a value of 3 marks.

BUILDING A SINGLE DECRYPTION CORE

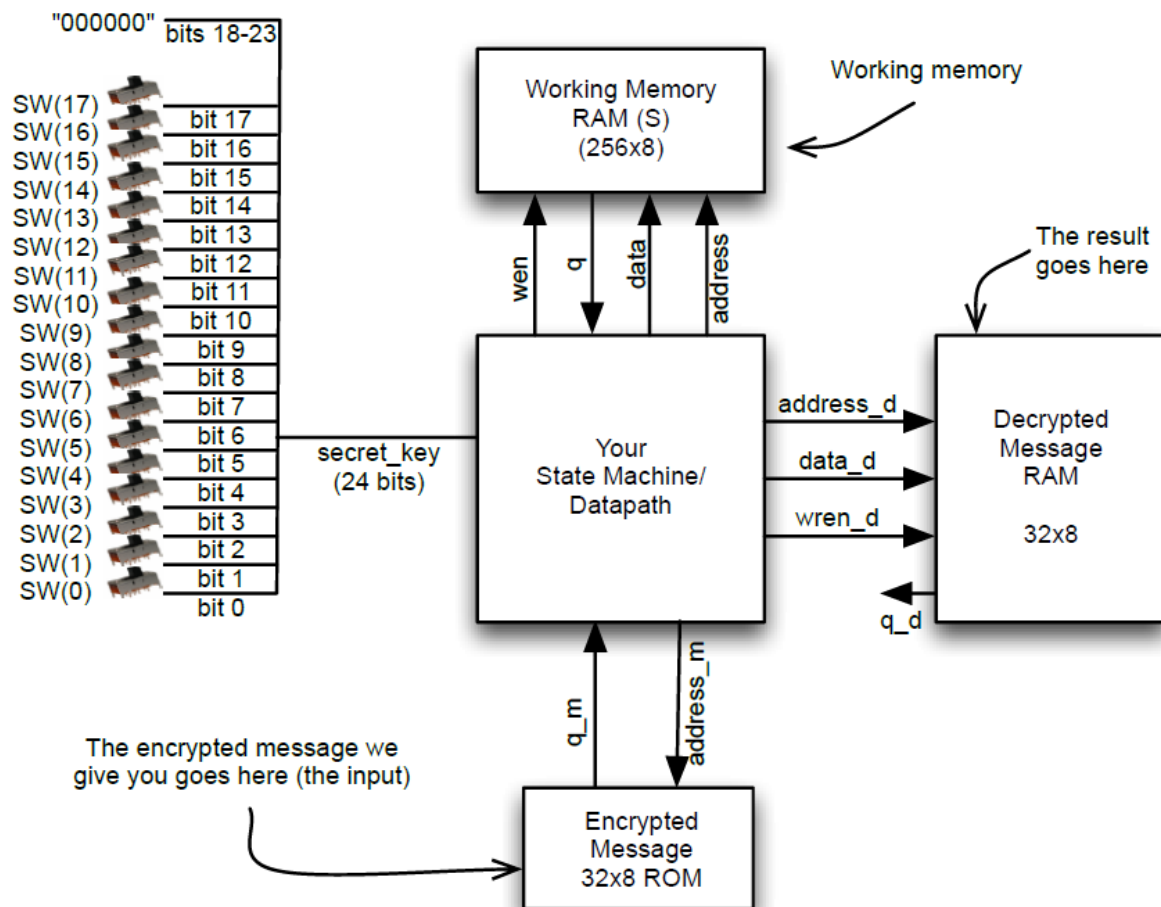TASK 2: you are to continue your design from Task 1 to implement a single decryption core. Given a *24 bits* key, and an encrypted message in a ROM, your algorithm will decrypt the message and store the result in another memory. You will then use the *In-System Memory Content Editor* to read the result to ensure the encryption occurred as expected.

As shown below, your system will consist of three memories and a state machine/datapath. The initial encrypted message is stored in a 32-word ROM (which you will initialize using a **.mif** file when you compile the design). The result is stored in a 32-word RAM (which you can examine using the *In-System Memory Content Editor* after the decryption is complete. In addition, you will use a 256x8 bit S memory. The secret key is set using the slider switches. Note that the secret key should be 24 bits long, but you only have 18 slider switches on the DE2 board. Therefore, you can hardwire the upper order six bits of the secret key to 0.:



Second Loop in algorithm

Starting with your Task 1 code, add hardware to implement the second loop from the algorithm on the second page of this handout. That is, add code to implement

```

j = 0
for i = 0 to 255 {
    j = (j + s[i] + secret_key[i mod keylength] ) mod 256
    //keylength is 3 in our impl. swap values of s[i] and s[j]
}
    
```

- Set the secret key to 00000011 01011111 00111100 = x035F3C (remember you can set the lower order 18 bits of secret key using the slider switches as in the above diagram)
- Examine the **S** array using the in-system memory content editor as before.

```

000000 03 63 A1 C6 65 48 42 C2 59 00 75 54 6A 68 79 34 FA 47 41 25 .c..eHB.Y.uTjhy4.GA%
000014 13 D0 D2 11 8C 90 82 09 39 1C EF 0A C9 DD D1 B9 F4 52 DA 1B .....9.....R..
000028 06 C7 CB A7 21 3C FD 36 05 4E 46 67 2B 80 9F CC F3 C4 C5 EE ...!<.6.NfG+>C.D
00003c 97 20 60 73 30 31 B7 66 85 DE 7E FE 02 5A 5E AC 57 E0 1D 44 . `s0l.f.~..Z^.W..D
000050 28 12 78 AA 04 BF F9 58 A0 EC 08 A4 56 9A 5C DB 84 EA 9C 64 (.x...X...V.\....d
000064 99 8D 1F 7C D7 D6 C3 70 16 A9 A6 62 BD E5 F2 B3 E9 76 01 88 ...|...p...b....v..
000078 CE 35 98 53 CA FF 0E FB B5 45 E6 38 43 A3 51 18 32 3F 3D B0 .5...S.....E.8C.Q.2?=.
00008c 5F A8 95 40 6F AE 72 29 9E AD C3 89 C8 4C B1 2C BE BA 9D AF ..@o.r)...3..L,...
0000a0 6D 4A D9 7D C1 3E D8 D5 27 2E C0 B4 93 4D 19 7A CF 3A FC 5D mj.}>.>.'...M.z.~.]
0000b4 A5 50 A2 49 BB 61 E3 24 6B 15 74 E7 0B B8 6C 4B 81 10 3B E1 .P.I.a.$k.t...lK.~;.
0000c8 96 DA 4F 26 69 77 1E 2D 0D 6E B2 EB 86 9B 7B 2F 8F CD 22 91 ..0&iw.-.n....{/..".
0000dc F0 8E 7F D3 94 DC F8 ED E2 F6 BC E4 DF 0F 17 1A F5 8B 5B 0C .....Ug....#*.7..
0000f0 AB E8 8A B6 07 55 71 14 92 87 23 2A F7 37 83 F1 .....Ug....#*.7..

```

Now, you will complete the rest of the algorithm (the third for loop in the pseudo-code on Page 1 of this handout). This will require adding two memories: one to store the encrypted message (this could be a ROM since the message to decrypt will be compiled with your hardware) and one to store the decrypted message (this could be a RAM since your circuit must write the result to it). To create the ROM and RAM, it is suggested that you use the *Wizard* (as you did for Task 1).

Test your design.

```
000000 74 68 69 73 20 63 6F 75 72 73 65 20 69 73 20 6D 79 20 66 61  this course is my fa
000014 76 6F 75 72 69 74 65 20 20 20 20 20      vourite
```

Finally, you may see this common error: Watch out for a warning such as:

*Critical Warning (127003): Can't find Memory Initialization File or Hexadecimal (Intel-Format) File
./db/message mod.mif -- setting all initial values to 0*

If you see this warning, it did not find your **message.mif** file during compilation. Make sure it is in your project directory, and that you specified it properly when you made your component.

Marks

This section will have a value of 8 marks.

CHALLENGE TASK

Not a specific task, but rather the complete and correct execution of all components of this design will grant you this mark. No compilation errors and Code well commented will also be considered.

Marks

This section will have a value of 1 mark.

WHAT TO DEMO

You don't need to demo each component individually. For this laboratory, it is suggested to demo the complete system and then go into details. Test several examples and get ready to show them to your TA. Modify variables to test different cases.

In all cases, for full marks, you must demo your working circuit on the FPGA board (simulation or on paper/code explanation will not suffice).

Remember to always:

- Have support material to explain the operation of your code (State Machine diagrams, Logic blocks diagrams, commented code, previous ModelSim result graphs, etc.).
- Get a backed up fully operational code copy in case any corrupted file or unexpected situation happens to your original files.
- Be certain of how your device operates and how to explain its operation so that full marks could be achieved.
- Use additional hardware resources to make your implementation easier to explain (LEDs to show changes or events, input accepted, others), mostly for FMS.

If you got the entire design working, demonstrate that to the TA and submit all VHDL files.

Your code must be submitted no later than 24 hours after your demo. You must ensure you submit exactly the code that you demoed; submitting code other than the code you demo is considered academic misconduct.

You should submit all of the .vhd files that you have written. Please do not zip up your entire working directory and submit it; if everyone does this, it takes too much space. Only submit the .vhd files. Do not submit temporary files, or .vhd files that you did not modify.

Finally, a reminder that **all team members must be present** to demo the operation of your design (**if one person is not present, that person will not receive marks for this lab**).